

Lecture 3

Integrated Electronics and Biopotential Measurements


Amplifier Properties: Ideal vs. Nonideal

	Gain (open loop)	Bandwidth (frequency response)	Input impedance (interfacing to sensors)	Output impedance (interfacing to load)	Noise ($\mu\text{V}/\sqrt{\text{Hz}}$ or $\mu\text{A}/\sqrt{\text{Hz}}$)	CMRR (diff/comm on mode gain)
Ideal	α	α	α	0	0	α
Nonideal	10 e 6	1 M Hz	100 Mohms	100 ohms	1 μV , 1 nA	100,000
Example	?	?	?	?	EEG	?

Operational Amplifier (OP AMP)

Basic and most common circuit building device. Ideally,

OPAMP

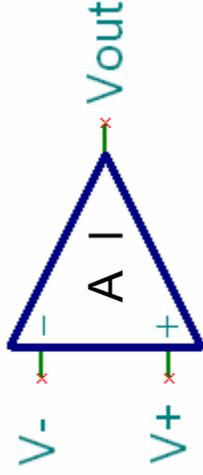

1. No current can enter terminals V_+ or V_- . Called *infinite input impedance*.


2. $V_{out} = A(V_+ - V_-)$ with $A \rightarrow \infty$

$$\begin{aligned} V_o &= (A V_+ - A V_-) \\ &= A (V_+ - V_-) \end{aligned}$$

3. In a circuit V_+ is forced equal to V_- . This is the *virtual ground* property

4. An opamp needs two voltages to power it V_{cc} and $-V_{ee}$. These are called the *rails*.

Input Impedance

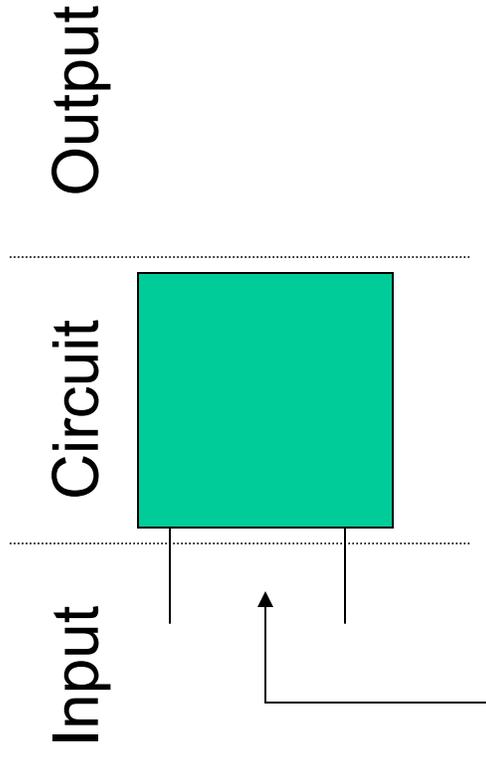

Impedance between
input terminals = input
impedance


WHY?

For an instrument the Z_{IN} should be very high (ideally infinity) so it does not divert any current from the input to itself even if the input has very high resistance.

e.g. an opamp taking input from a microelectrode.

Output Impedance

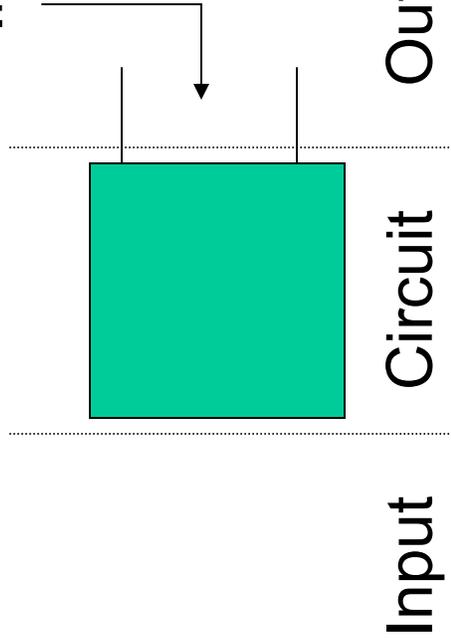Impedance between output terminals =
output impedance




WHY?

For an instrument the Z_{OUT} should be very low (ideally zero) so it can supply output even to very low resistive loads and not expend most of it on itself.

e.g. a power opamp driving a motor

OPAMP: Comparator

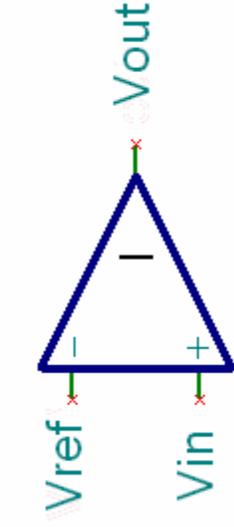


$$V_{out} = A(V_{in} - V_{ref})$$

If $V_{in} > V_{ref}$, $V_{out} = +\infty$ but practically hits +ve power supply = V_{cc}

A (gain)
very high

If $V_{in} < V_{ref}$, $V_{out} = -\infty$ but practically hits -ve power supply = $-V_{ee}$

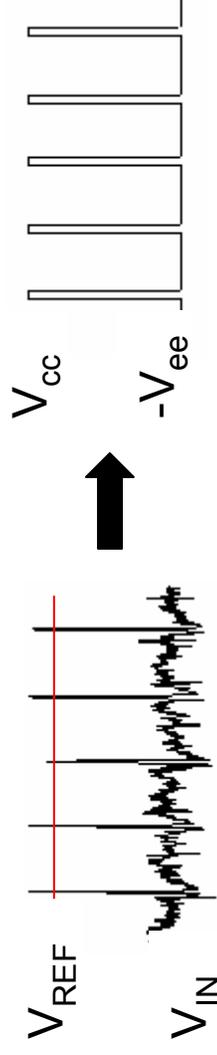Application: detection of QRS complex in ECG




OPAMP: Analysis

The key to op amp analysis is simple

1. No current can enter op amp input terminals.
=> Because of infinite input impedance
2. The +ve and -ve (non-inverting and inverting) inputs are forced to be at the same potential.
=> Because of infinite open loop gain
3. These property is called “virtual ground”
4. Use the ideal op amp property in all your analyses

OPAMP: Voltage Follower

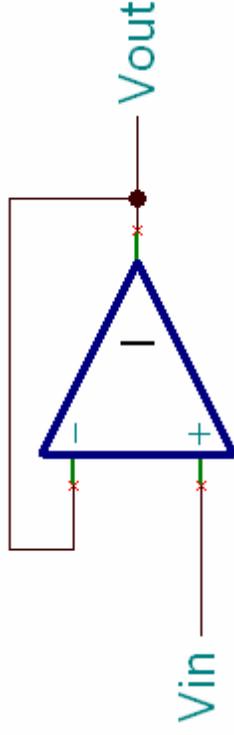

$$V_+ = V_{IN}$$


By virtual ground, $V_- = V_+$

Thus $V_{out} = V_- = V_+ = V_{IN}$!!!!

So what's the point ? The point is, due to the infinite input impedance of an op amp, no current at all can be drawn from the circuit before V_{IN} . Thus this part is effectively isolated.

Very useful for interfacing to high impedance sensors such as microelectrode, microphone...

OPAMP: Inverting Amplifier

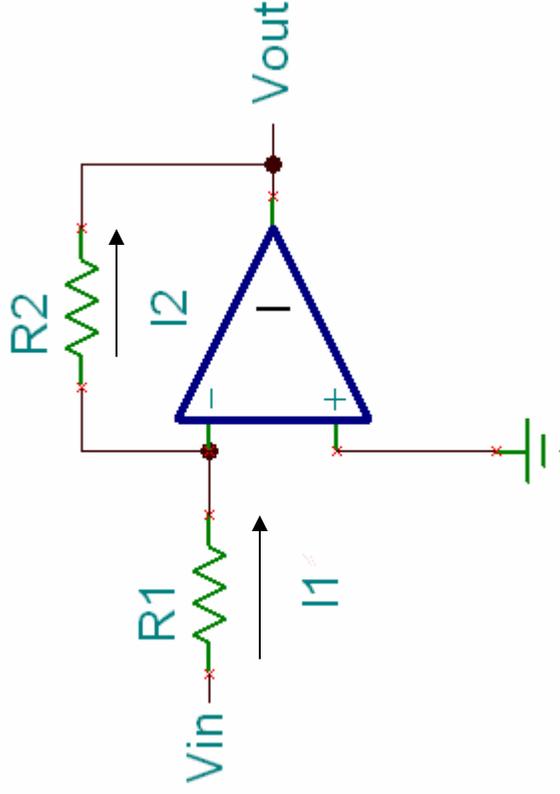

1. $V_- = V_+$

2. As $V_+ = 0$, $V_- = 0$

3. As no current can enter V_- and from Kirchoff's 1st law, $I_1 = I_2$.


4. $I_1 = (V_{IN} - V_-)/R_1 = V_{IN}/R_1$

5. $I_2 = (0 - V_{OUT})/R_2 = -V_{OUT}/R_2 \Rightarrow V_{OUT} = -I_2 R_2$

6. From 3 and 5, $V_{OUT} = -I_2 R_2 = -I_1 R_2 = -V_{IN}(R_2/R_1)$

7. Therefore **$V_{OUT} = (-R_2/R_1)V_{IN}$**

OPAMP: Non-Inverting Amplifier

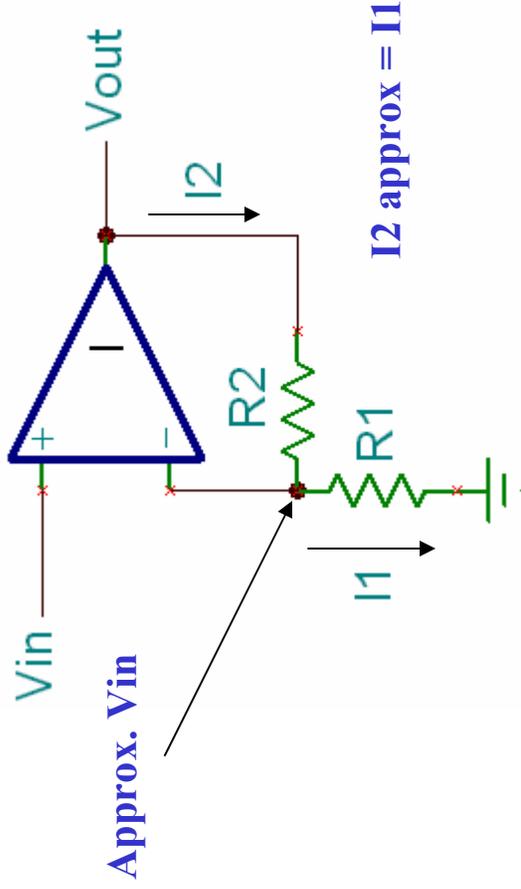

1. $V_- = V_+$

2. As $V_+ = V_{IN}$, $V_- = V_{IN}$

3. As no current can enter V_- and from Kirchoff's 1st law, $I_1 = I_2$.


4. $I_1 = V_{IN}/R_1$

5. $I_2 = (V_{OUT} - V_{IN})/R_2 \Rightarrow V_{OUT} = V_{IN} + I_2 R_2$

6. $V_{OUT} = I_1 R_1 + I_2 R_2 = (R_1 + R_2) I_1 = (R_1 + R_2) V_{IN} / R_1$

7. Therefore $V_{OUT} = (1 + R_2/R_1) V_{IN}$

Differential Amplifiers

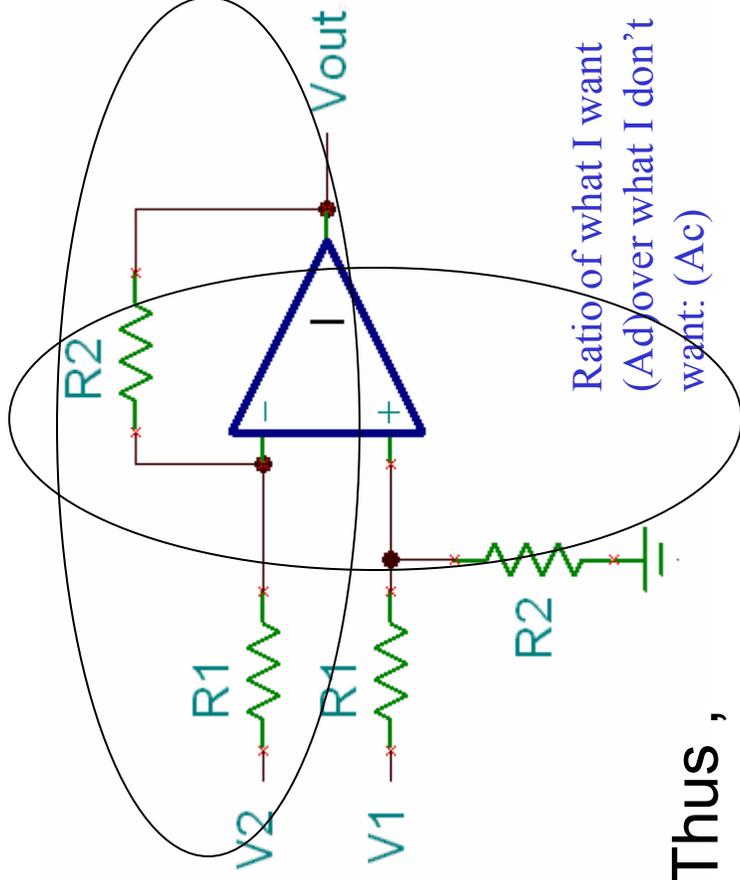

$$V_{\text{OUT}} = (V_1 - V_2)R_2/R_1$$

Amplifies a *difference*.

Common noise sources add symmetrically to an opamp. Thus there is a differential ($V_1 - V_2$) and a common mode ($V_1 + V_2$) component to the input.


Thus ,

$$V_{\text{OUT}} = A_C(V_1 + V_2) + A_D(V_1 - V_2)$$

A_D : differential (signal) gain, A_C : common mode (noise) gain.

The ratio A_D/A_C (Common Mode Rejection Ratio – CMRR) is a very important parameter. Ideally CMRR $\rightarrow \infty$

Summing Amplifier

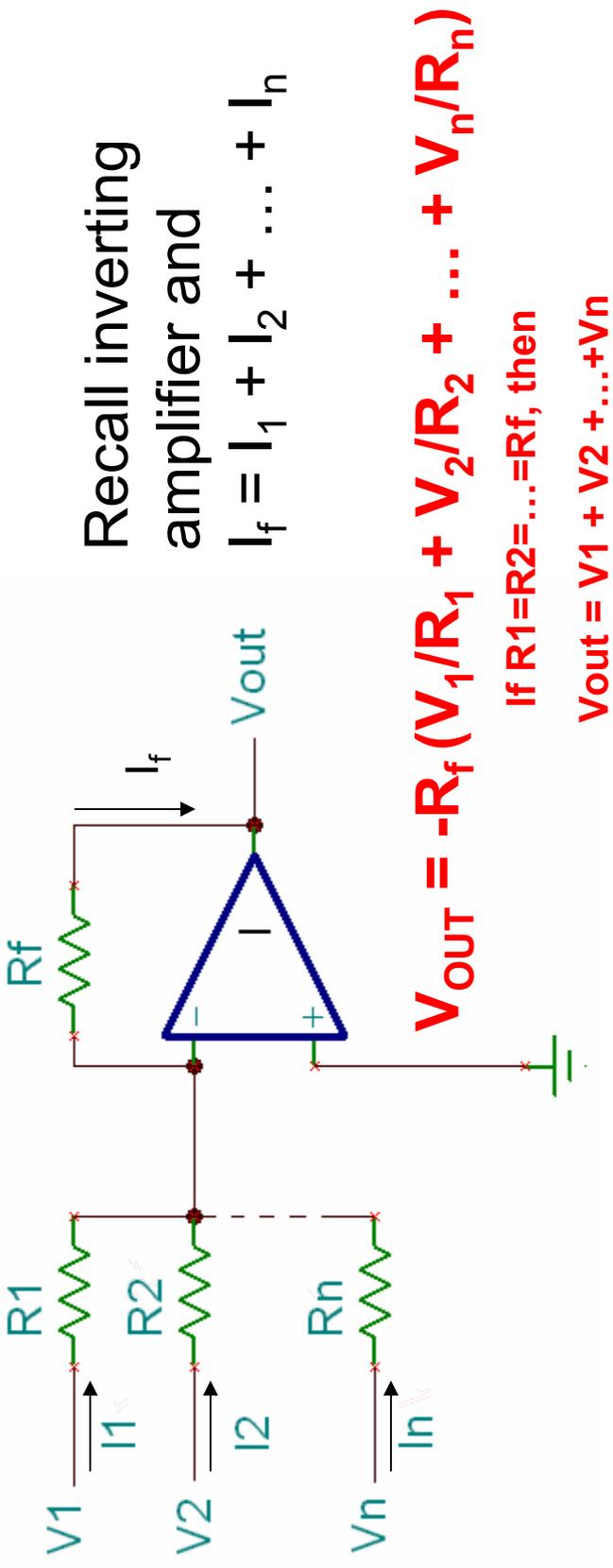


Summing amplifier is a good example of analog circuits serving as analog computing amplifiers (analog comps!)

Note: analog circuits can add, subtract, multiply/divide (using logarithmic components, differentiate and integrate – in real time and continuously.


Driving OPAMPS

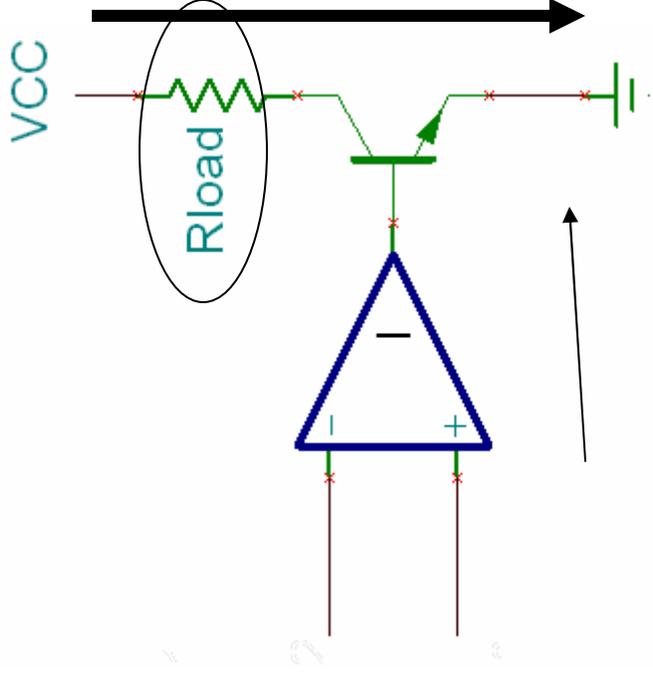
For certain applications (e.g. driving a motor or a speaker), the amplifier needs to supply high current. Opamps can't handle this so we modify them thus



Irrespective of the opamp circuit, the small current it sources can switch ON the BJT giving orders of magnitude higher current in the load.


We would like to measure small displacements or strains using strain gauges. These are variable resistances that respond to small changes in strain/stretch-contraction of the surface the sensor is mounted on. (i) suggest a suitable application. (ii) A useful design is to put the strain gauge in a bridge circuit design. Calculate the output of the following circuit for a very small dR changes with respect to the R values of the bridge elements. Hint: The output should be a relationship between V , R , dR , R_f and V_o .

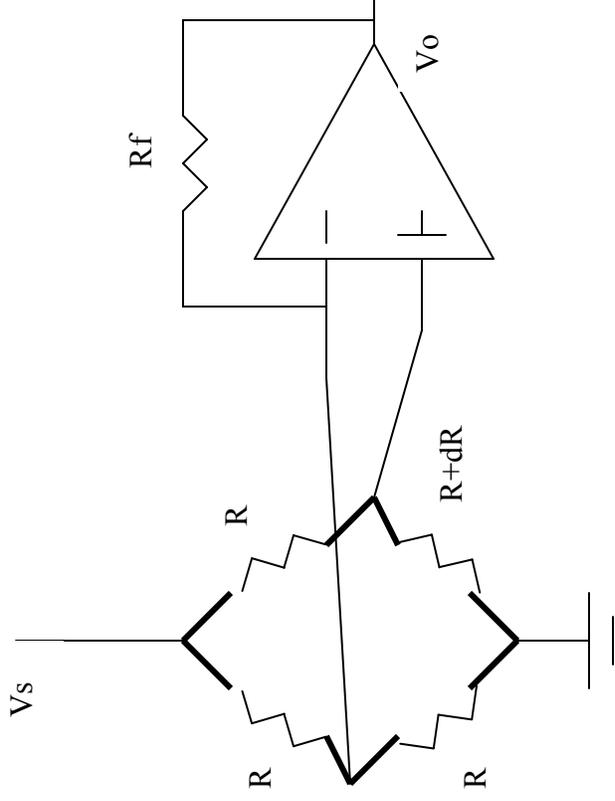

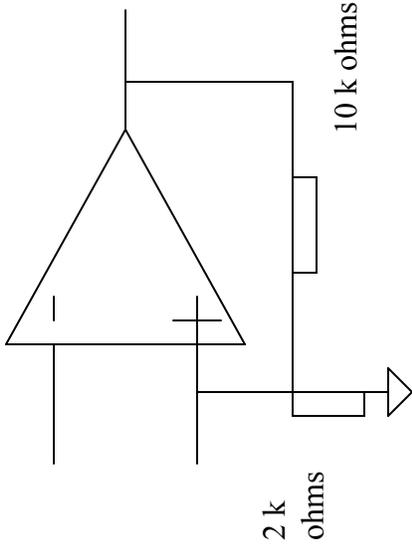


This is a circuit of a comparator (note the positive feedback). What would be the output of this circuit for the following input voltages: -5 V , -1 V , $+1\text{ V}$, and $+5\text{ V}$? The op amp is powered by $\pm 10\text{ V}$ (that would also be the maximum swing of the output).


You visit a hospital and see a state of the art ECG monitoring instrument. You open up the technical manual and the following circuit is presented to you. Ostensibly, this circuit is at the output of the ECG amplifier (i.e. the amplified ECG goes to this circuit) and the output (marked ?) goes to a comparator. $C = 1\text{ }\mu\text{F}$ and $R = 330\text{ k}\Omega$. Draw the signal you expect to see at the point marked by a question mark.

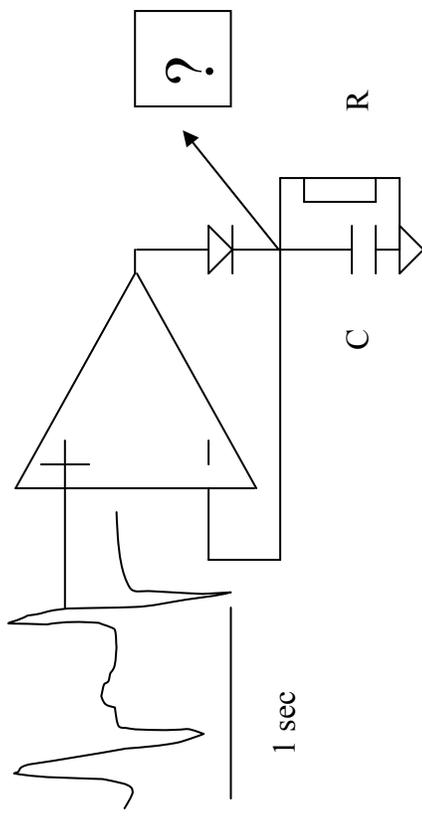

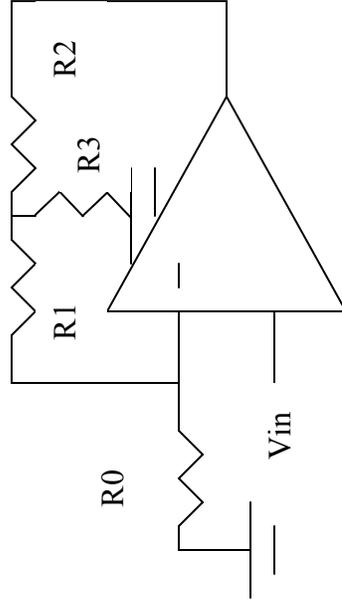For the following circuit, what is the input impedance and the output impedance.
Now, calculate the closed loop gain. Use basic circuit analysis ideas using op
amps to work through the analysis (Hint: identify the virtual ground, obtain
currents in the input and the feedback paths, obtain input-output relationship).




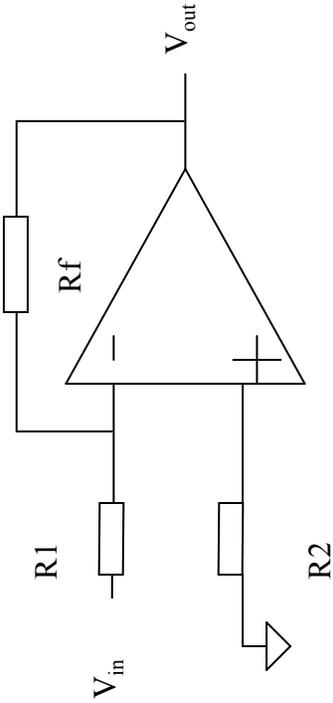For the following circuit, calculate the input resistance. (i) First, calculate input resistance for an ideal amplifier. (ii) Next, calculate the input resistance of a non-ideal amplifier. Note that the input resistance of the op amp is R_{in} (not shown, but you can assume such a resistance going to ground from each of the $-$ and $+$ inputs).



Instrumentation Amplifier

Inverting amplifier

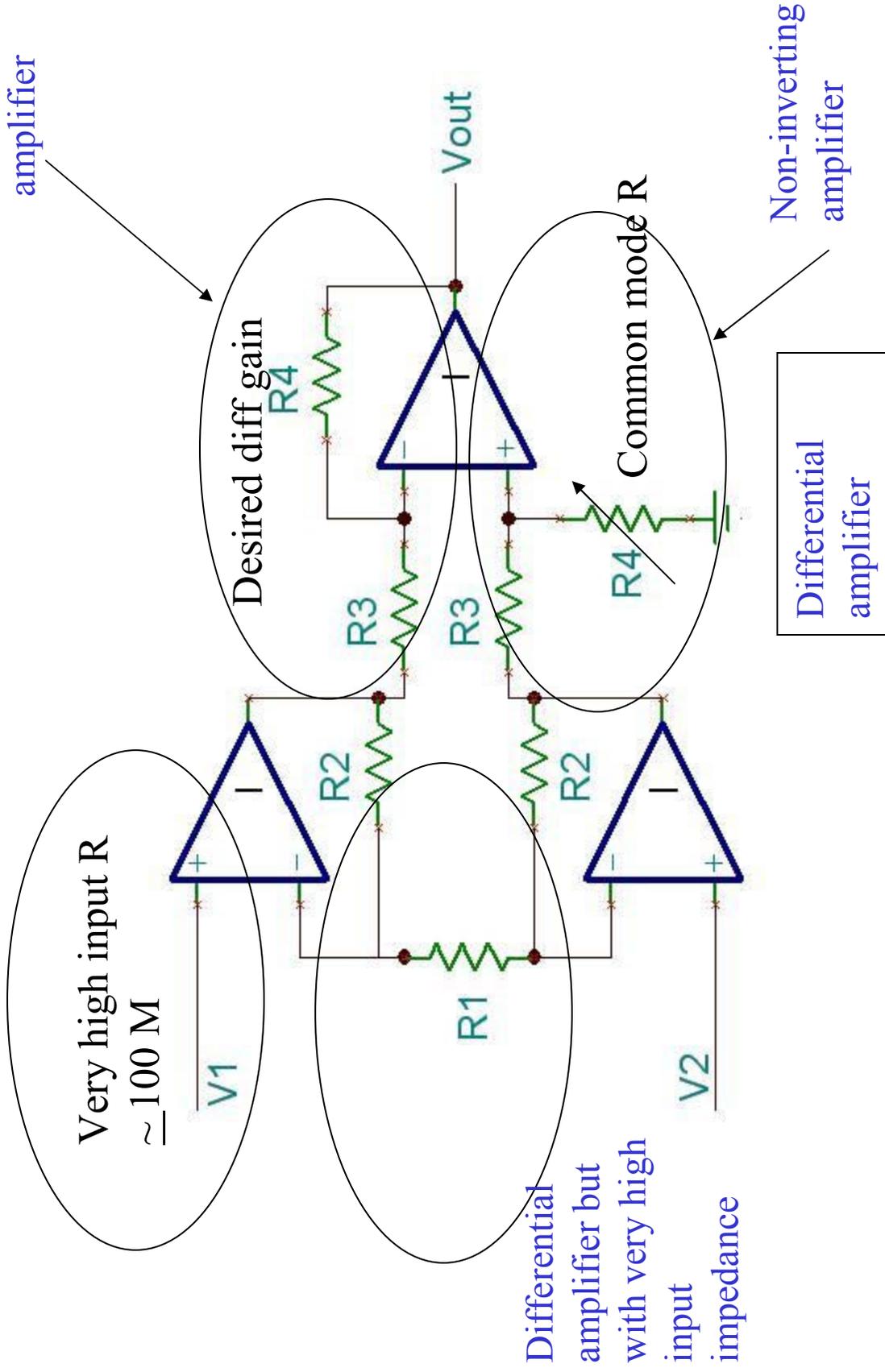

Instrumentation Amplifier: Stage 1

Recall virtual ground of opamps


$$I_1 = (V_1 - V_2)/R_1$$

Recall no current can enter opamps and Kirchoff's current law


$$I_2 = I_3 = I_1$$

Recall Kirchoff's voltage law
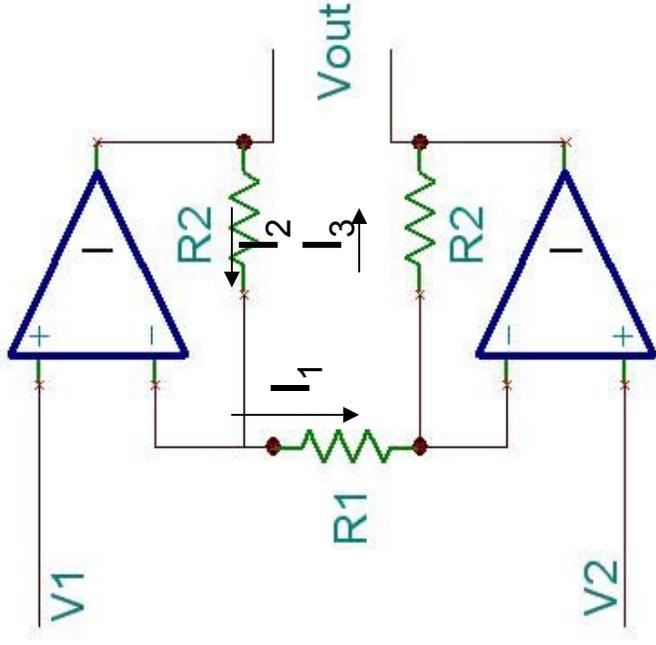
$$\begin{aligned} V_{\text{OUT}} &= (R_1 + 2R_2)(V_1 - V_2)/R_1 \\ &= (V_1 - V_2)(1 + 2R_2/R_1) \end{aligned}$$



Instrumentation Amplifier: Stage 2

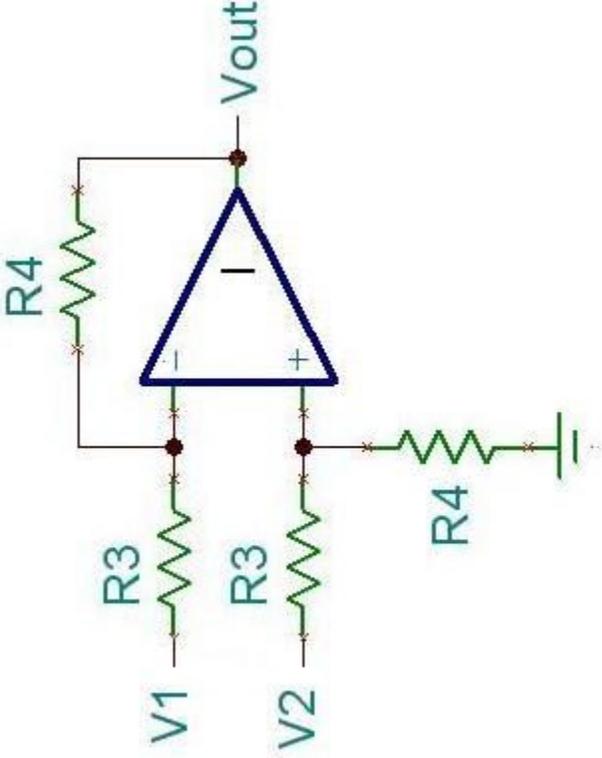

Recall virtual ground of opamps
and voltage divider

$$V_- = V_+ = V_2 R_4 / (R_3 + R_4)$$


Recall no current can enter opamps

$$(V_1 - V_-) / R_3 = (V_- - V_{OUT}) / R_4$$

Solving,

$$V_{OUT} = - (V_1 - V_2) R_4 / R_3$$


Instrumentation Amplifier: Complete

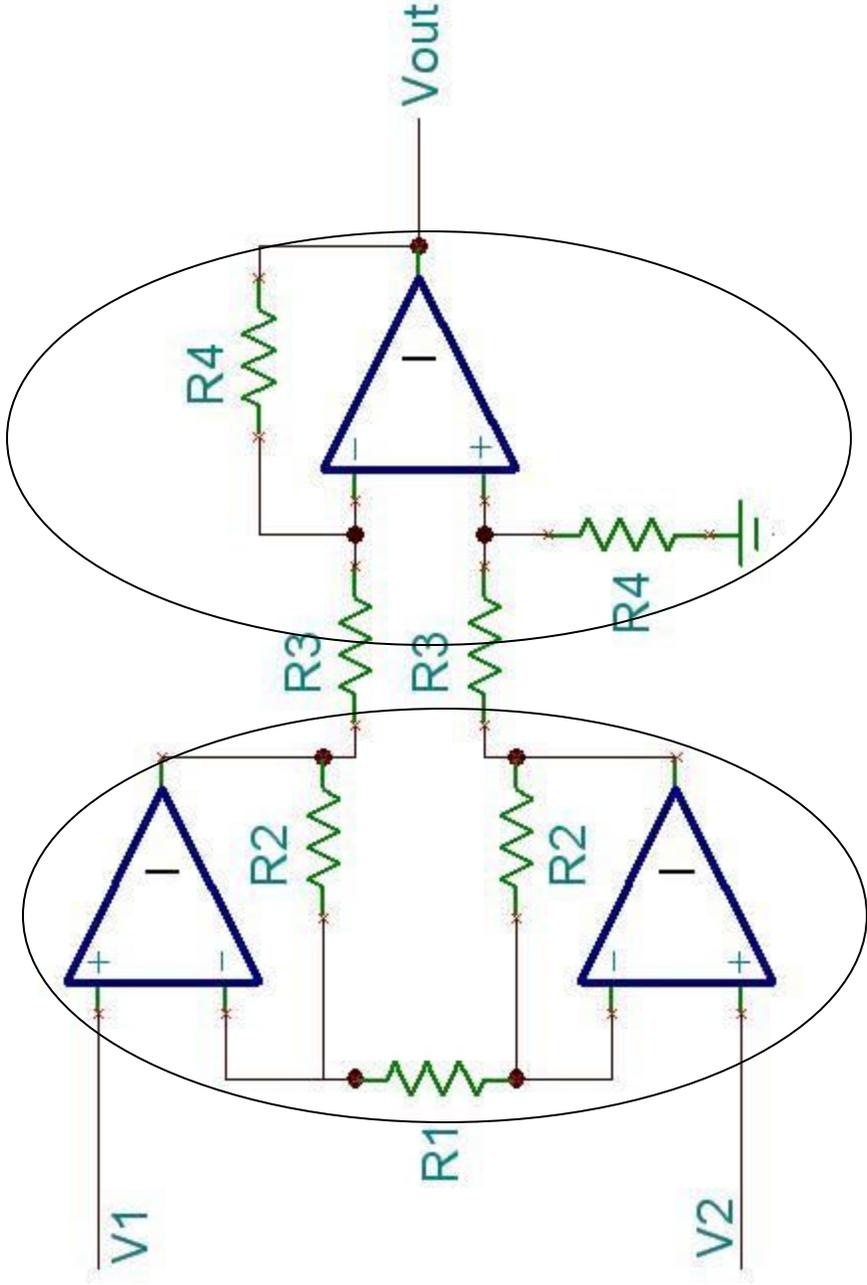

$$V_{OUT} = -(V_1 - V_2)(1 + 2R_2/R_1)(R_4/R_3)$$

↔ Gain from Stage I and Stage II

Instrumentation Amplifier: Complete

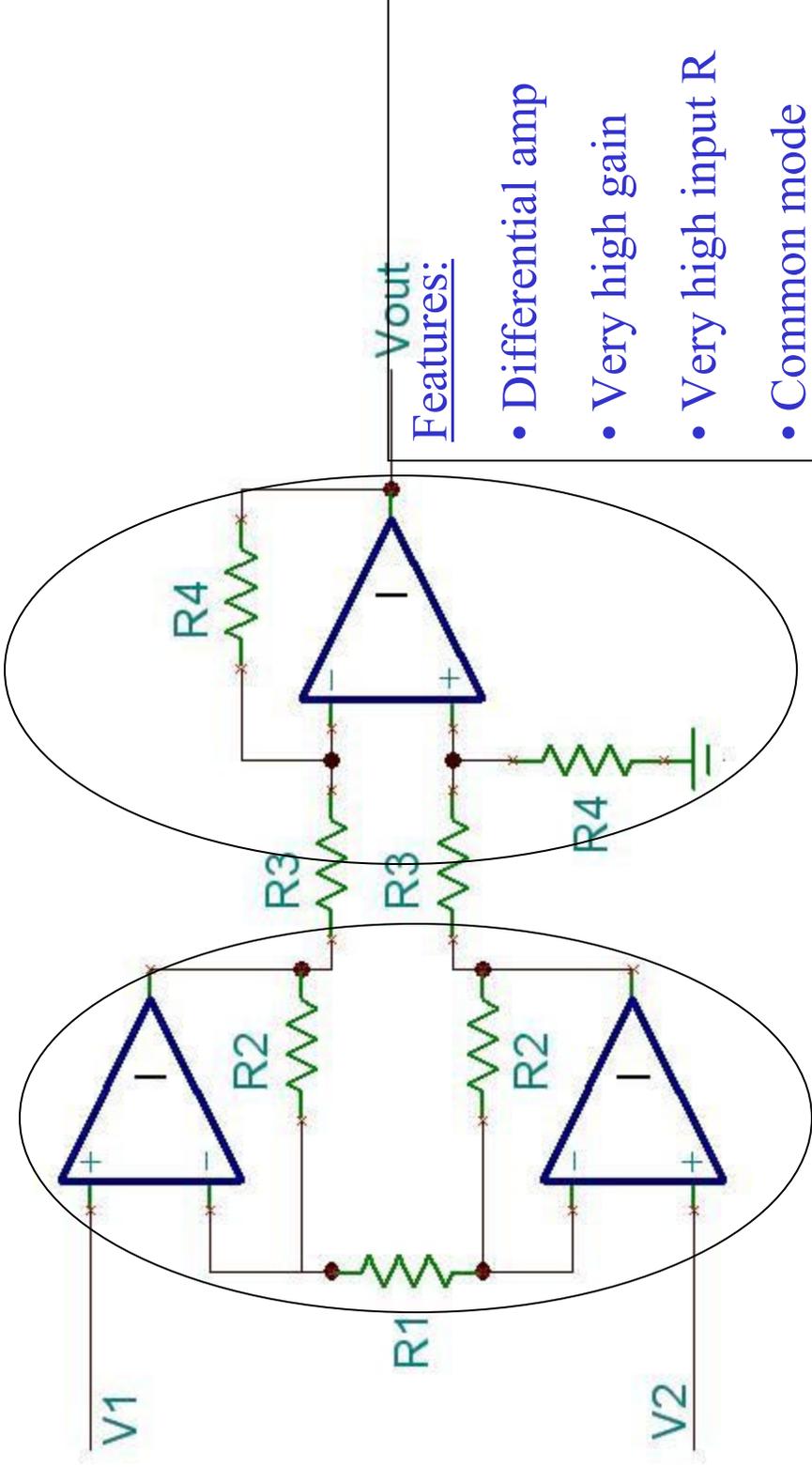

$$V_{OUT} = -(V_1 - V_2)(1 + 2R_2/R_1)(R_4/R_3)$$

↔ Gain from Stage I and Stage II

Features:

- Differential amp
- Very high gain
- Very high input R
- Common mode rejection
- we also need filters

ECG: Einthoven's Triangle

Leads I, II, III

- Three vectors used to fully identify the electrical activity
 - vector shown in frontal plane of the body
- Kirchhoff's law is used for the three leads

$$I - II + III = 0$$

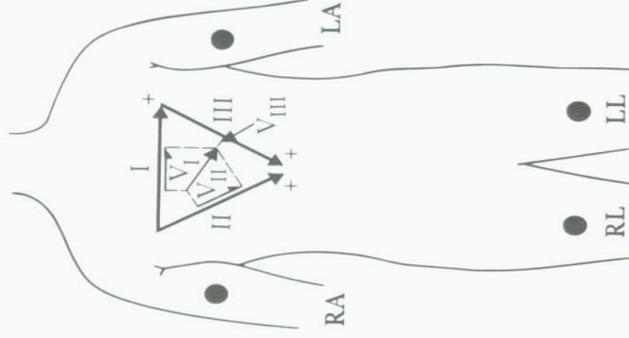


Figure 6.3 Cardiologists use a standard notation such that the direction of the lead vector for lead I is 0° , that of lead II is 60° , and that of lead III is 120° . An example of a cardiac vector at 30° with its scalar components seen for each lead is shown.

ECG: Electrode Placement

Augmented

leads:

aVR, aVL, aVF

Right, left, foot

With respect to
central terminal

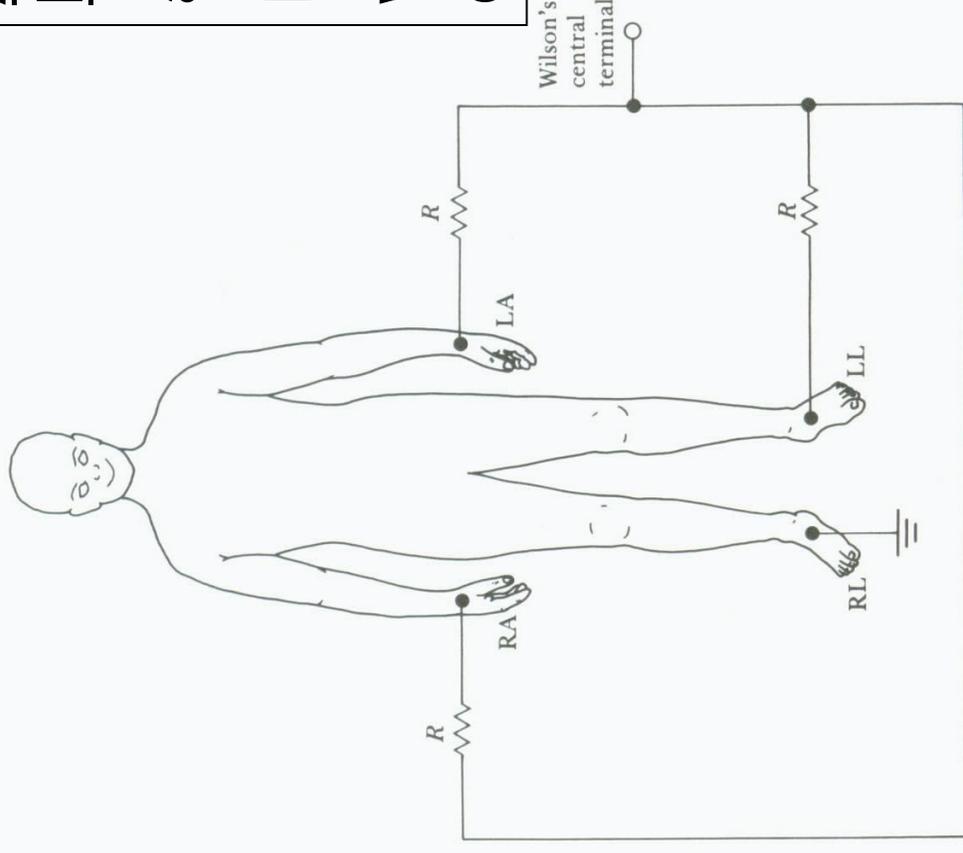


Figure 6.4 Connection of electrodes to the body to obtain Wilson's central terminal

ECG: Transverse Plane

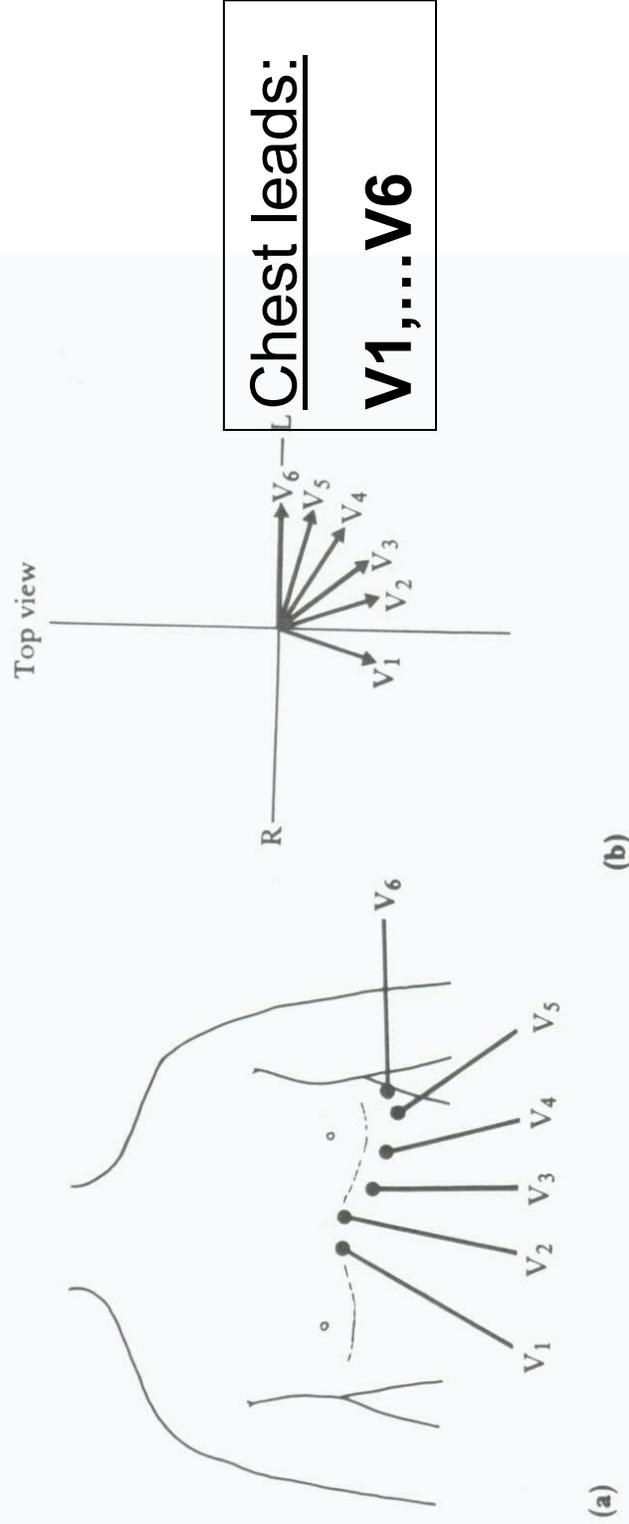


Figure 6.6 (a) Positions of precordial leads on the chest wall. (b) Directions of precordial lead vectors in the transverse plane.

- Chest leads used to obtain the ECG in the transverse plane;
- Obtains ECG from the posterior side of the heart
- All together: 12 leads (**I,II,III; aVR, aVL, aVF, V1... V6**)



Frequencies of Biopotentials

Signal	Frequency range (Hz)	Amplitude range(mV)
ECG	0.01 – 100	0.05 – 3
EEG	0.1 – 80	0.001 – 1
EOG	0.01 – 10	0.001 – 0.3
EMG	50 – 3000	0.01 – 100

Why Frequency?

When measuring biopotentials (say ECG), EVERYTHING else matters

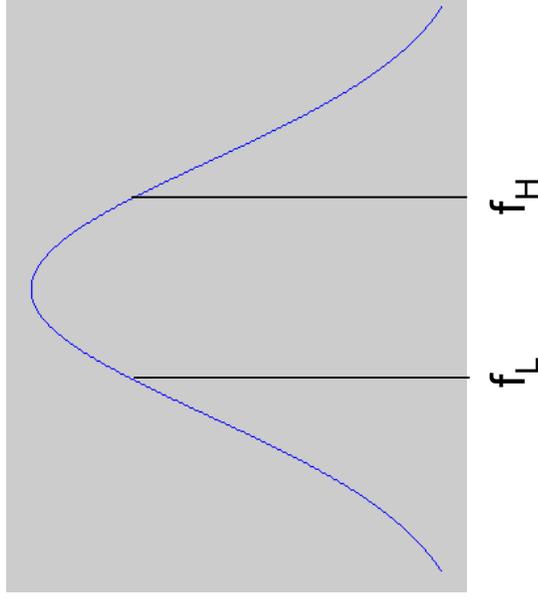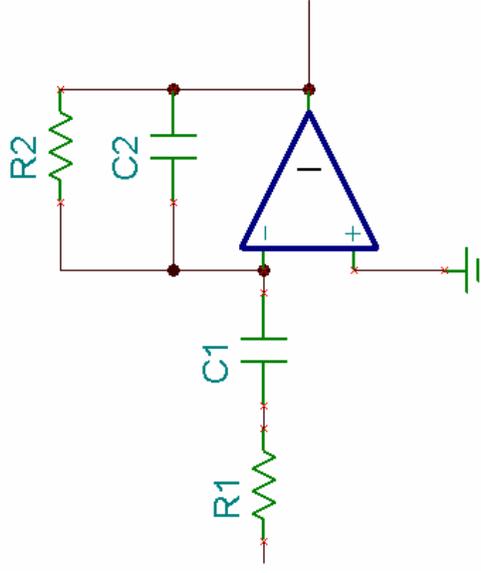- power line interference
- even other biopotentials (like EEG, EMG, EOG) are noise sources. These have characteristic frequencies. So use Band Pass Filters.




Pass only f_L to f_H attenuate the others.

Noise

- Several sources
 - 60Hz power lines – *shielding, filtering*
 - *(and harmonics; also RF or radio frequencies)*
 - Other biopotentials
 - *e.g. EOG in EEG or EMG in ECG*
 - Motion artifacts – *relaxed subject*
 - Electrode noise – *high quality electrodes, good contacts*
 - Circuit noise – *good design, good components*
 - Common mode noise – *differential design, high CMRR*


Safety

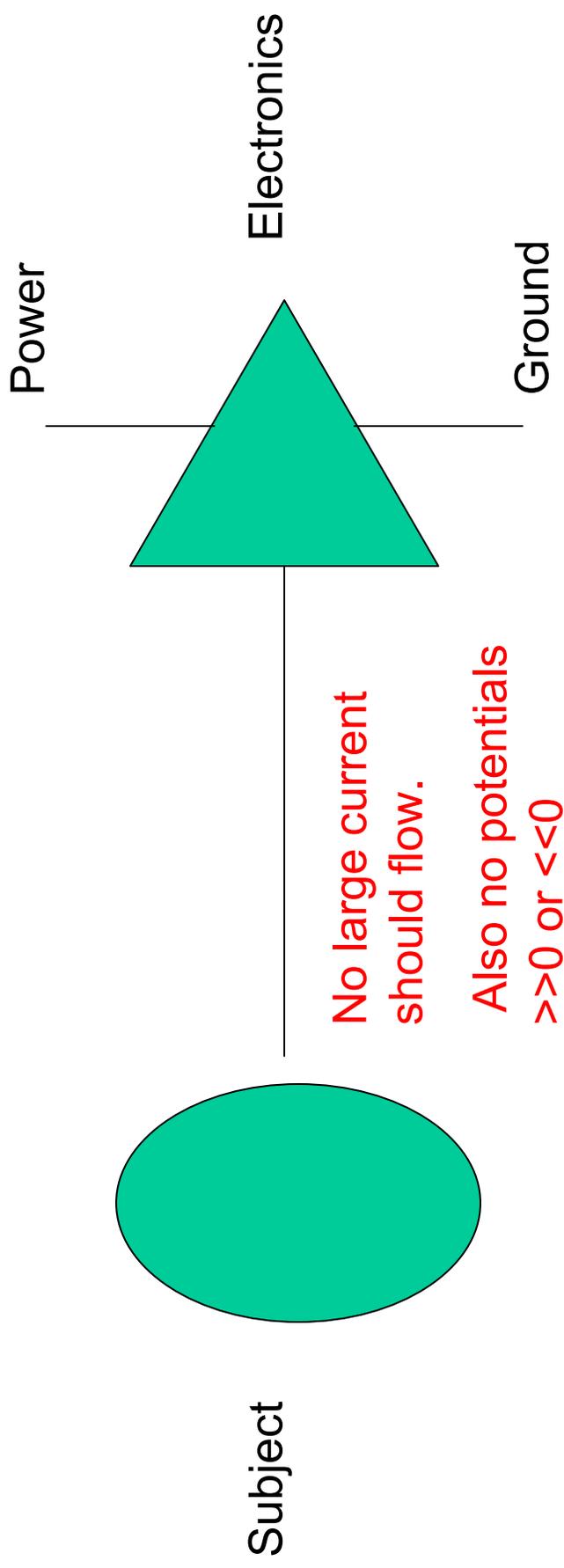- Amplifiers are powered, should not shock or electrocute the subject




Safety: Protection Circuits

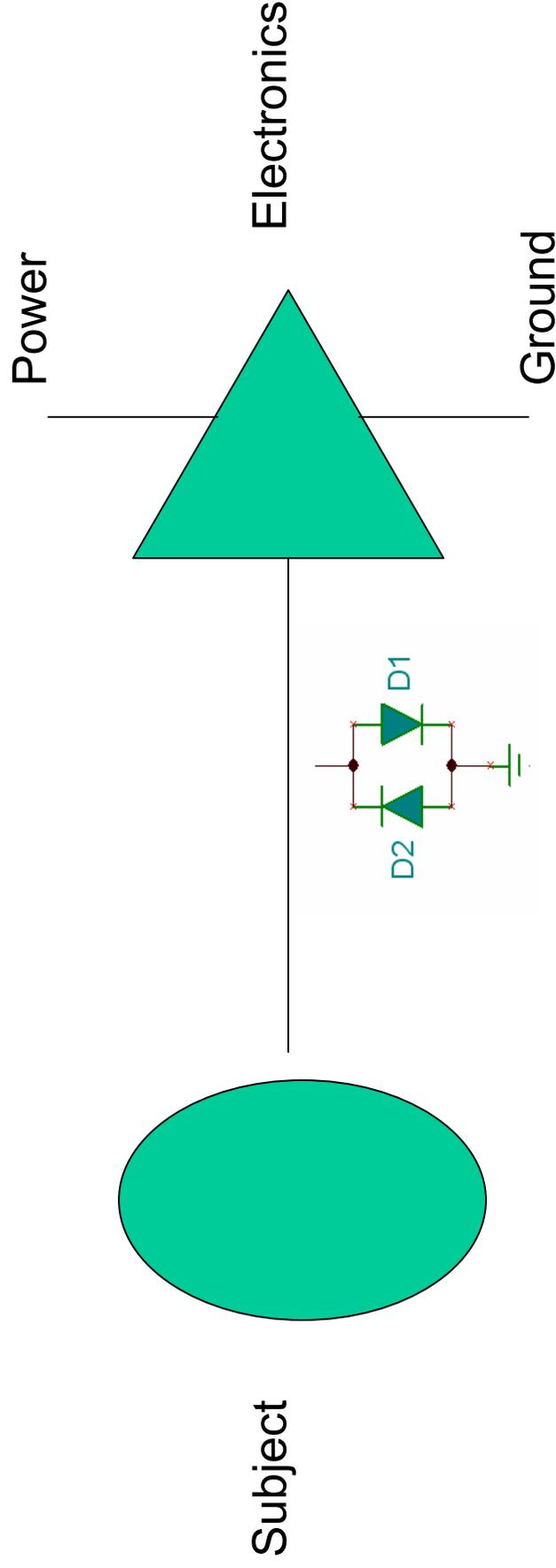- If potential >0 , high current grounded through D1
- If potential <0 , high current grounded through D2



Safety: Isolation

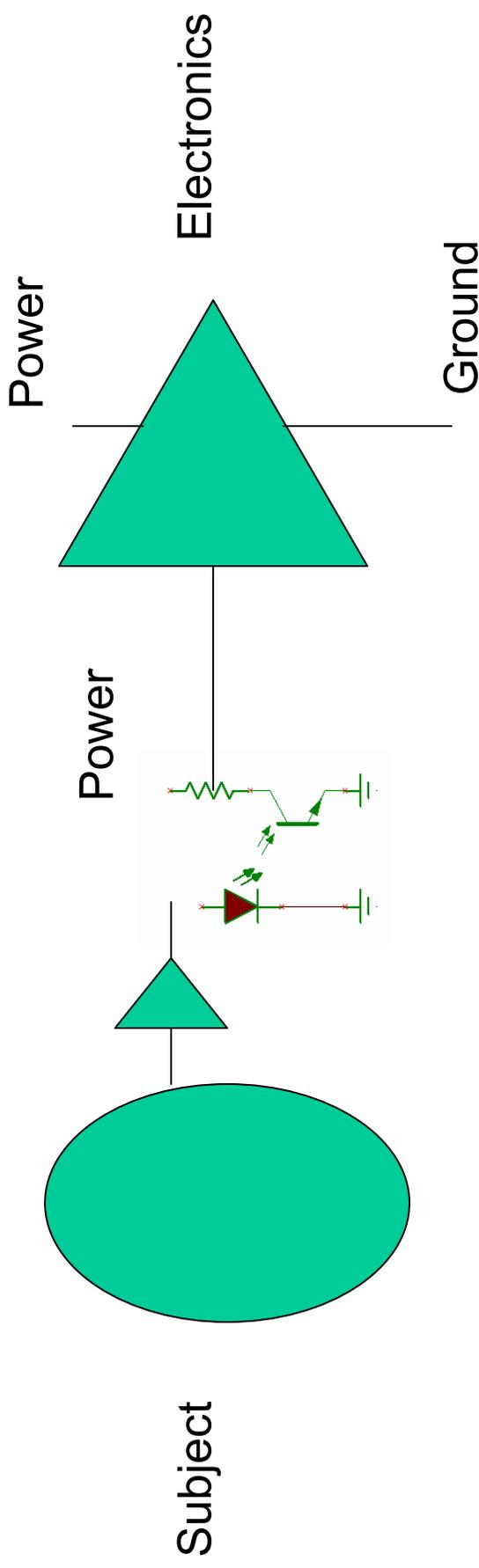
- Potential transferred through optoelectronics (shown), transformers etc.
- Circuits are electrically isolated, no current leakage



Electricity -> Light -> Electricity → Provides electrical isolation



Telemetry

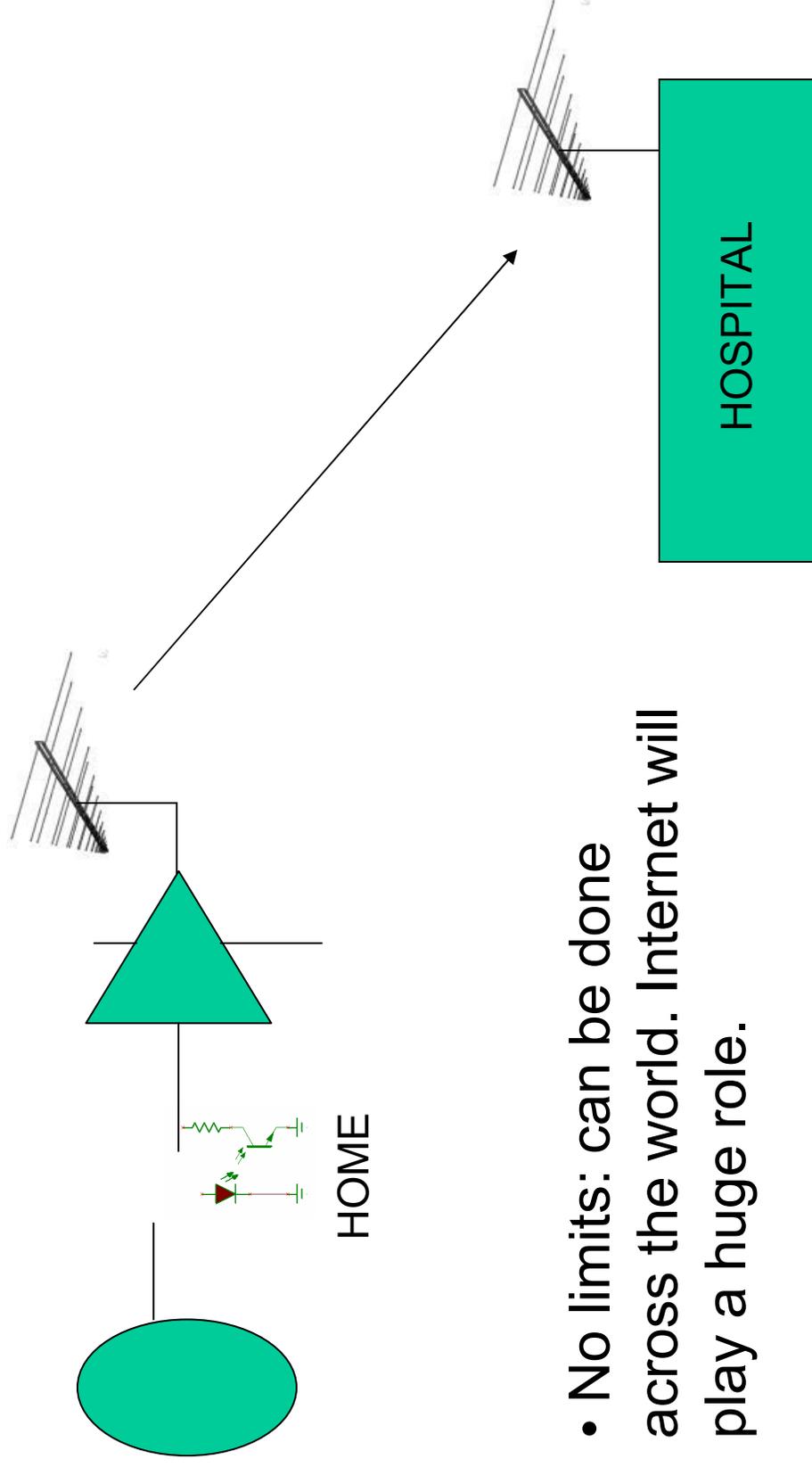- Means wireless transmission of data from and to the device




- No limits: can be done across the world. Internet will play a huge role.

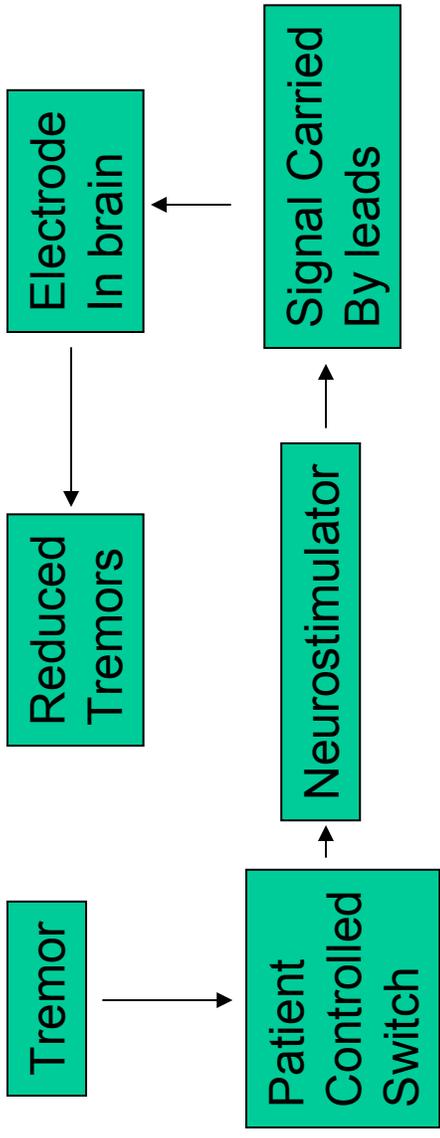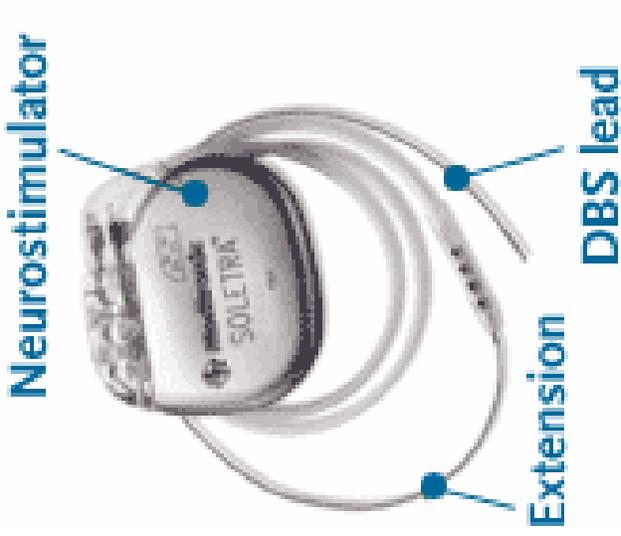APPLICATION: Neurostimulator System by Medtronic for Parkinson's Disease



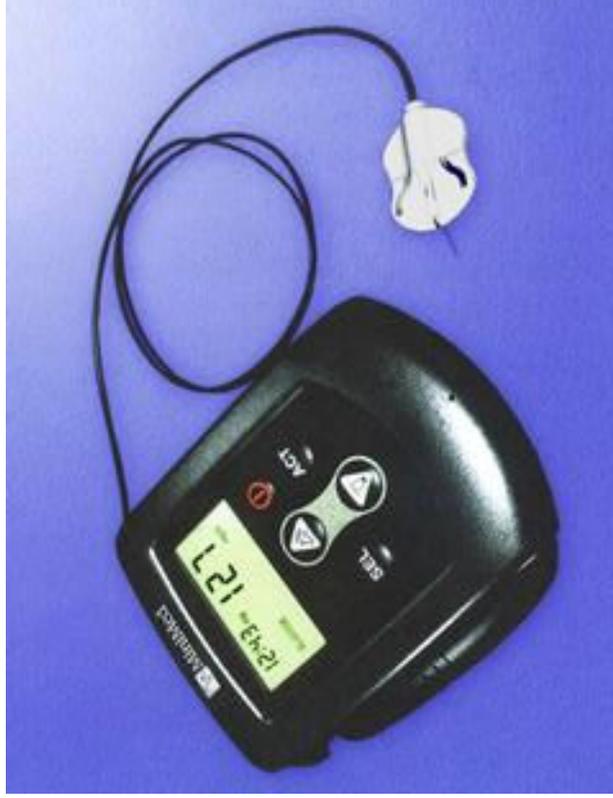
APPLICATION: Medtronic MiniMed Continuous Glucose Monitoring System



- Sensor inserted subcutaneously into abdomen.
- Connected to small pager-sized monitor (worn by patient)
- Continuous reading for up to 3 days to determine direction or trend of blood glucose levels.

APPLICATION: Fetal ECG

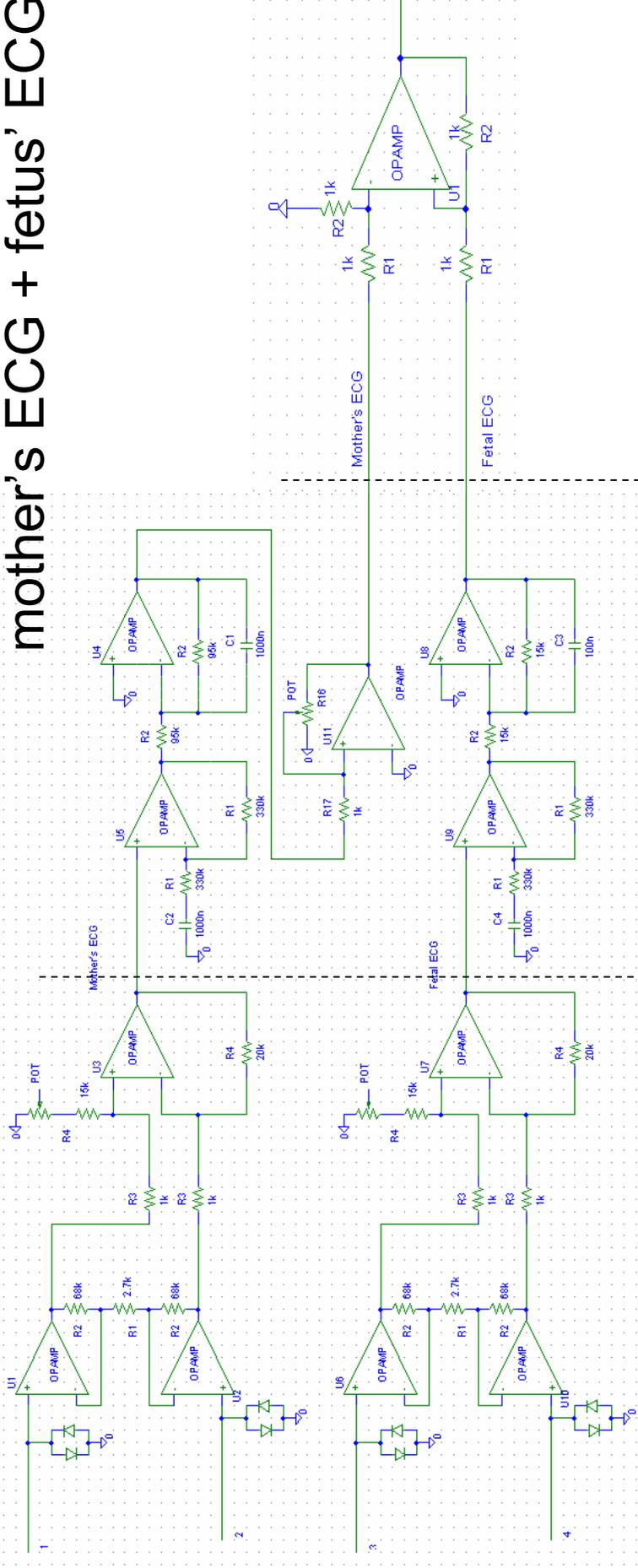Problem: Recorded ECG =
mother's ECG + fetus' ECG



UP: mother ECG ampl.


DN: fetus ECG ampl.

mother ECG filters

fetus ECG filters

$$V_{OUT} = \text{mother's ECG} - \text{fetus' ECG}$$

APPLICATION: Gastric Pacemaker

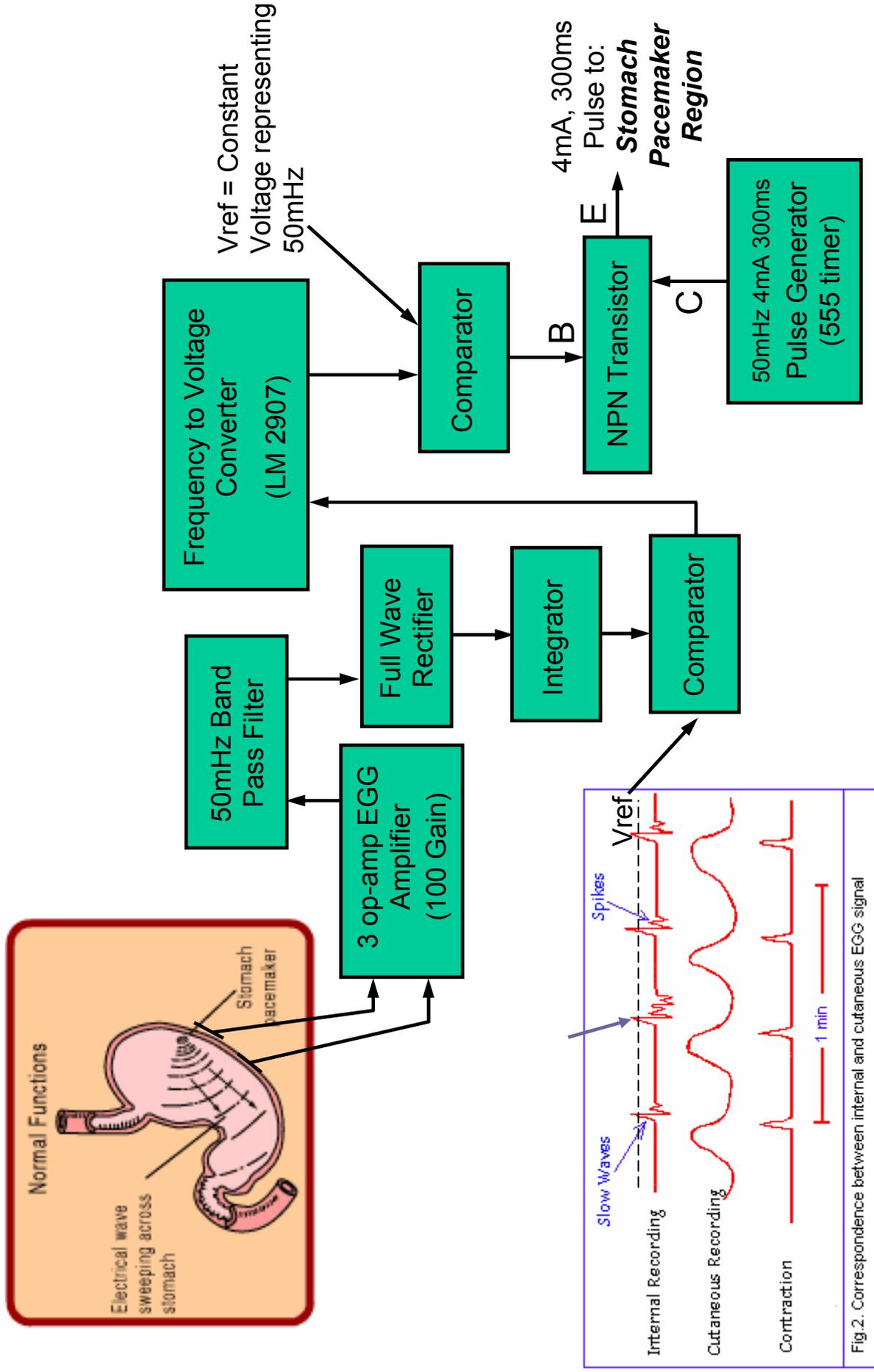

Problems

1. This question reviews the design issues for an ECG amplifier used in monitoring a patient in an operating room or an intensive care.
 - (a) What are the sources of high voltage hazards? How should the amplifier be protected? Draw a protection circuit.
 - (b) It is essential that the patient be further protected from leakage currents and other hazards from the instrument being connected to power and ground. Describe two alternate designs of amplifier isolation. Draw at least one of them in a circuit form.
 - (c) Besides the amplifier itself, list what else goes into making a full bed-side ECG monitor. You may also add “bells and whistles” to make your device more marketable. Now, itemize and estimate the cost of different materials, features, and other business-related activities that industry would add on to come up with the final instrument cost.

2. Now let us design an ECG amplifier for the pacemaker. You know how to design an ECG amplifier. Modify it for use in a pacemaker. What should be the key features or specifications for an “implanted system?”
- a) For an implanted amplifier that goes in a pacemaker, what will be the sources of electrical interference? How should these interferences be minimized or rejected ?
 - b) Design and draw a small circuit to detect the heart beat pulse (do not draw or design ECG amplifier; give only the pulse detection circuit).
 - c) Research and draw an implanted pacemaker lead. Distinguish unipolar from bipolar leads.

3.1 Origins of Biopotentials, Sources and Field Modeling

The ECG signal generating from the heart can be modeled quite simply as a dipole. If a cardiac dipole has a magnitude of 1 mV and orientation of -45° with respect to Lead I, then calculate, using the Einthoven triangle, the magnitude of the signal in Lead I, II, and III. Show the geometric presentation as well as the trigonometric calculations.

What does the 12-lead ECG system comprise of (sketch the different leads)? Is it superior or inferior to an orthogonal system (X, Y, and Z leads)?

What kind of a lead system would you use to record EEG from the scalp and for localizing the source of epileptic seizure? Sketch it.

What instrument is used to measure the magnetic field from the brain?

B) What are the possible advantages and disadvantages of the magnetic versus electrical measurement? C) To your knowledge, what breakthroughs in the scientific world that have occurred (or ought to occur?) that would make magnetic field measurement more feasible and affordable? D) If you had a cheap magnetic field sensor (with a relatively lower sensitivity) available what other biomedical application would you think of (other than biopotential measurements).

Show (draw) the possible current distribution between an electrosurgical electrode, body and the return ground electrode. What would be the desirable properties of the ground reference electrode?

3.2 Origins of Biopotentials, Sources and Field Modeling

Imagine it is the beginning of the 20th century. Cardiac activity is suspected as an electrical source inside the torso. Let us say that you were a contemporary of Prof. Einthoven. Prof. Einthoven recommends that to record ECG from the torso using a triangular formulation with what you now know at three leads, I, II, and III (respectively LA-RA, RA-LL, and LA-LL). However, you claim have a different theory of better presenting the cardiac vector on a different lead system (for example, you prefer not to use 3 leads arranged in the form of a triangle). Demonstrate superiority of your lead idea.

After Einthoven's original idea, a number of solutions were suggested. One of these was to put 6 leads (V1-V6) around the left ventricle. a) why around left ventricle? b) for the 6 differential amplifiers, each with one input being V1.. V6 what is the other "neutral" input source?


Einthoven came up with the idea of creating a triangle to come up with an experimental interpretation of the cardiac vector. In one measurement, we recorded a 5 mV signal in Lead II and 3 mV signal in lead III. (a) Calculate the Lead I signal magnitude. (b) Calculate the cardiac vector. (Hint: you may do this geometrically using the Einthoven's equilateral triangle or you may do this by calculating the vector (x, y components).

3.3 Origins of Biopotentials, Sources and Field Modeling

What instrument is used to measure the magnetic field from the brain? B) What are the possible advantages and disadvantages of the magnetic versus electrical measurement? C) To your knowledge, what breakthroughs in the scientific world that have occurred (or ought to occur?) that would make magnetic field measurement more feasible and affordable? D) If you had a cheap magnetic field sensor (with a relatively lower sensitivity) available what other biomedical application would you think of (other than biopotential measurements).


We would like to record ECG of a fetus while in the womb. The main problem here is that when electrodes are placed on the mother's stomach to capture the fetal ECG, a large maternal ECG signal pulse is also picked up. A) Draw a schematic of the mother and her heart dipole/vector and fetus and its heart dipole/vector. Now, show how mother's ECG might corrupt the fetal ECG. B) How would you eliminate the maternal ECG artifact from the stomach recording? C) Someone suggests that at the most critical moment in labor, as the head of the fetus presents itself first, attach the ECG electrode to fetal scalp. Would you succeed or not in getting fetal ECG from an electrode placed on the scalp and why/why not? D) During the time of the late stage labor, what would be more likely to succeed – electrodes on the mother's stomach or an electrode on fetus's head?

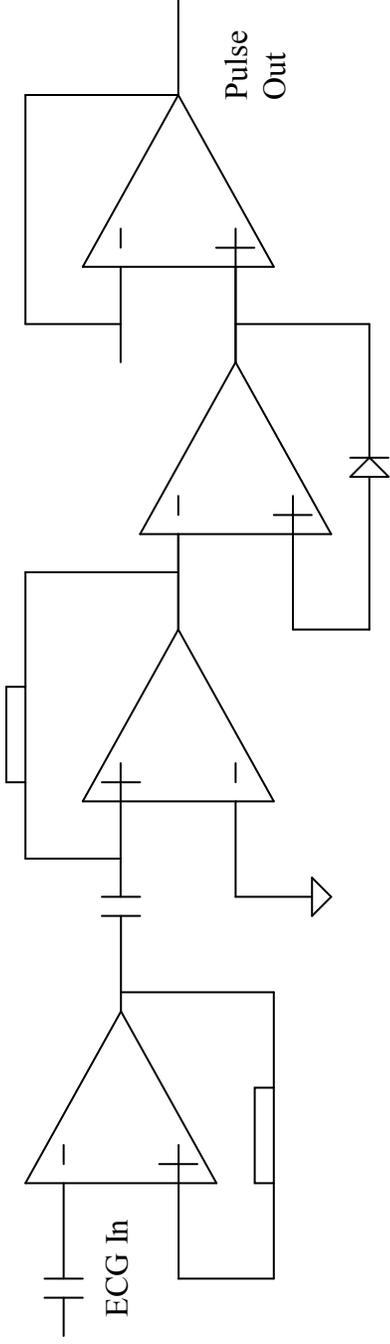4. You have already built an ECG amplifier. Now you want to build a heart beat (QRS pulse) detector. This design, consisting of a bandpass filter, rectifier and a comparator is sketched below. Unfortunately, there are several “mistakes” in this design. Please circle the mistakes and correct them.



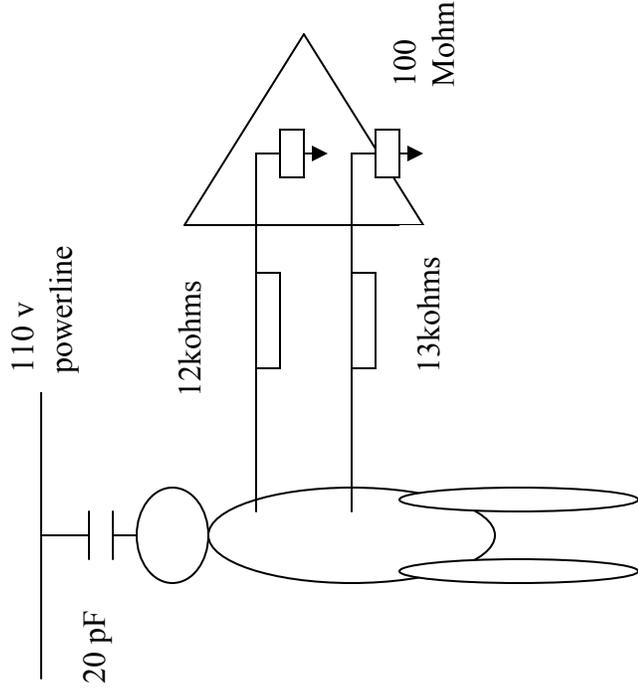
5.1 Electrical Interference Analysis

The following figure shows a person connected to an ECG amplifier via two electrodes with resistance of 12 and 13 kohms. The 110 powerline is coupled via a 20pF capacitance between the powerline and the subject. The input resistance of the amplifier is 100 Mohm (connected to ground). The student testing this set up forgets to connect the third, ground electrode on the subject.



Under the circumstances: a) what is the powerline induced current flowing into the subject? b) what is the common mode voltage produced at the amplifier input? c) What is the differential signal at the 60 Hz powerline signal?

5.2 Electrical Interference Analysis

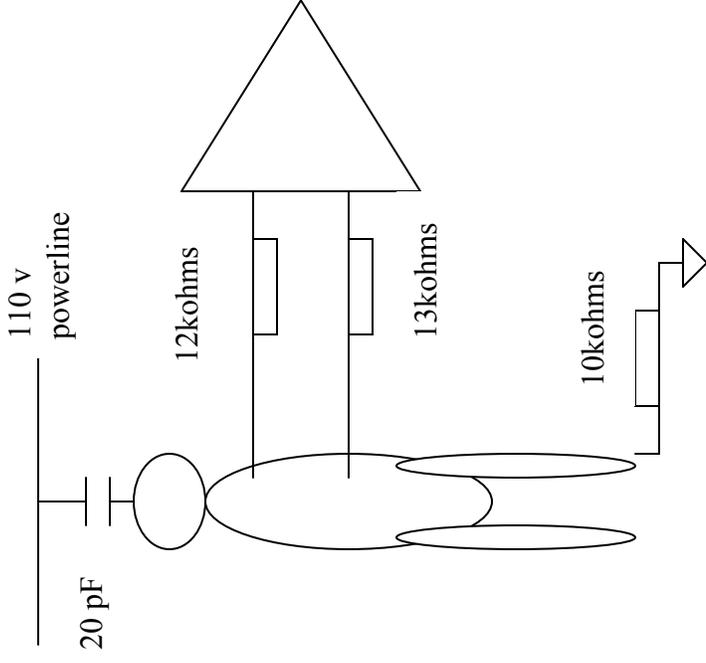

In the following schematic, what is the current induced into the subject (note that the powerline frequency is 60 Hz)? What is the common-mode voltage? What is the differential interference voltage resulting from the induced current (note that the amplifier input resistance is 100 Mohms)?

- A) If the environmental interference is 1 V, what is the CMRR needed to detect ECG signals? B) Derive the signal output when 1 mV differential and 1 V common mode signal are fed to an ECG amp with a CMRR of 10,000.